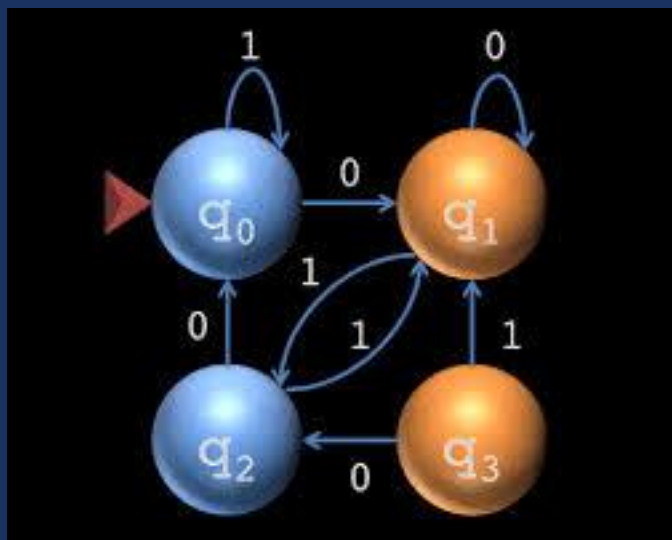




AUTOMATA WITH OUTPUTS

TRANSDUCERS




Syed Faisal Ali

faisal.ali@nu.edu.pk

Computer Science E & F

SPRING 2025

TRANSDUCER

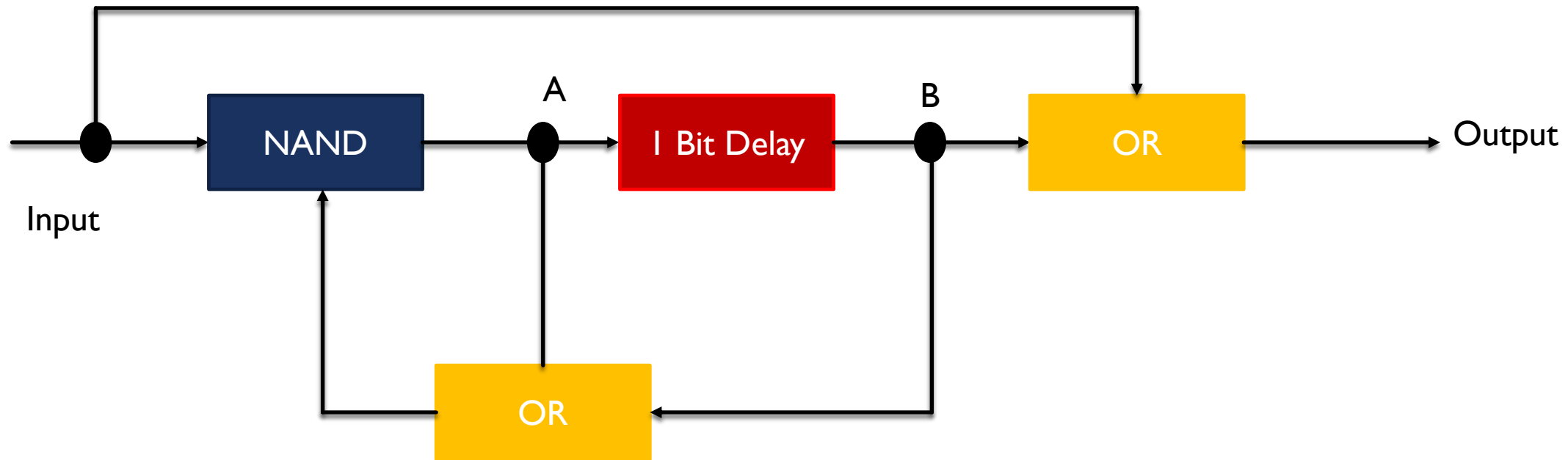

A **transducer** is a device or system that converts one form of input into another form of output. In the context of **automata theory and formal languages**, a **transducer** is typically a type of **finite automaton** that produces **output** along with processing **input**.

ANALYSIS

- In this transducer we can clearly found that some piece of information has already been given to us.
- Known as Parameters we known
- Also we need to find some of the parameters which we need to find consider as Unknown Parameters
- Before we start for input we know a clock 555 timer which can generate 0 and 1 as pulse train.
- For each 0 and 1 input the logical gates will generate some output which we can fill in the table to make Mealy or Moore Machine depending on our requirement.
- There are two nodes A and B from where we can change the states.

KNOWN PARAMETERS

- Input clock that generates 0 and 1.
- Node A and Node B for the combinations of [00, 01, 10, 11] which will be helpful for states, and consider as old states [q0, q1, q2, q3].
- Working of AND and OR logical gates
- 1 bit delay, means what ever the signal is at node A will be send to B in the next clock cycle.

UNKNOWN PARAMETERS

- Also we know the relationships as follows;
- New value of B will be old value of A due to DELAY means $NEW\ B = OLD\ A$
- $NEW\ A = (input)\ NAND\ (old\ A\ OR\ old\ B)$
- $Output = (input)\ OR\ (old\ B)$

STATES

- Now learn how we make the states:
 - We assume that $A=0$ and $B=0$, consider it as q_0 ,
 - When $A=0$ and $B=1$, consider it as q_1
 - When $A=1$ and $B=0$, consider it as q_2 ,
 - And When $A=1$ and $B=1$, consider it as q_3
-
- We are interested to find out what will be the next state so for that the input 0 and input 1.
 - We will input the clock pulse for each state and find the new states values

States	Node A	Node B
Q0	0	0
Q1	0	1
Q2	1	0
Q3	1	1

STRATEGY TO SOLVE

- Now we need to use the three formulas which we have extracted from the transducer.
- $\text{NEW B} = \text{OLD A}$
- $\text{NEW A} = (\text{input}) \text{ NAND } (\text{old A OR old B})$
- $\text{Output} = (\text{input}) \text{ OR } (\text{old B})$
- We use above three formulas and the values of old A and old B using this table to find the new values.
- By doing this we can get the values of output and next state switching.
- So we need to calculate individually for each state with input 0 once then with input 1.

Input	States	Value of old A	Value of old B
0	Q ₀	0	1
1	Q ₀	0	1
0	Q ₁	0	1
1	Q ₁	0	1
0	Q ₂	1	0
1	Q ₂	1	0
0	Q ₃	1	1
1	Q ₃	1	1

AT STATE Q0, WHEN $A = 0$ AND $B = 0$ AND INPUT = 0

new $B = \text{old } A = 0$

new $A = (\text{input}) \text{ NAND } (\text{old } A \text{ OR old } B)$


$= (0) \text{ NAND } (0 \text{ OR } 0)$

$= 0 \text{ NAND } 0$

$= 1$

output $= 0 \text{ OR } 0 = 0$

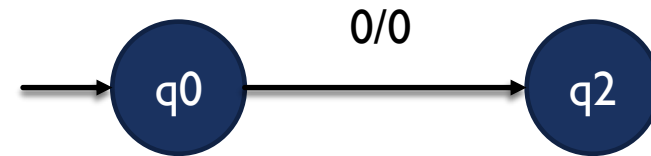The new state is q_2 (since new $A = 1$, new $B = 0$).




AT STATE Q0, WHEN $A = 0$ AND $B = 0$ AND INPUT = 1

new $B = \text{old } A = 0$

new $A = 1 \text{ NAND } (0 \text{ OR } 0) = 1$

output = $1 \text{ OR } 0 = 1$

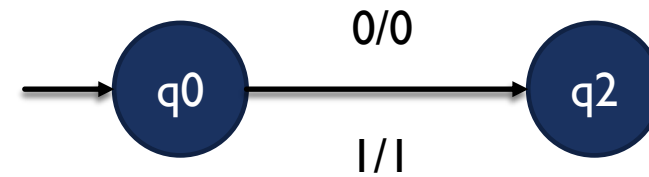The new state is q_2 (since the new $A = 1$ and the new $B = 0$).



AT STATE Q1, WHEN $A = 0$ AND $B = 1$ AND INPUT = 0


If we are in $q1$, and we receive the input 0:

new $B = \text{old } A = 0$

new $A = 0 \text{ NAND } (0 \text{ OR } 1) = 1$

output = $0 \text{ OR } 1 = 1$

The new state is $q2$.

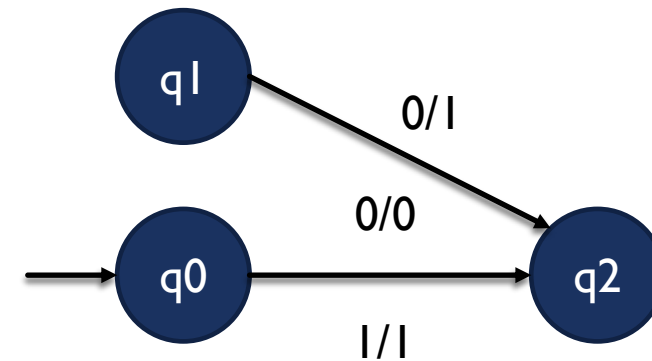

AT STATE Q1, WHEN $A = 0$ AND $B = 1$ AND INPUT = 1


If we are in $q1$, and we receive the input 1:

$\text{new } B = \text{old } A = 0$

$\text{new } A = 1 \text{ NAND } (0 \text{ OR } 1) = 0$

$\text{output} = 1 \text{ OR } 1 = 1$

The new state is $q0$.

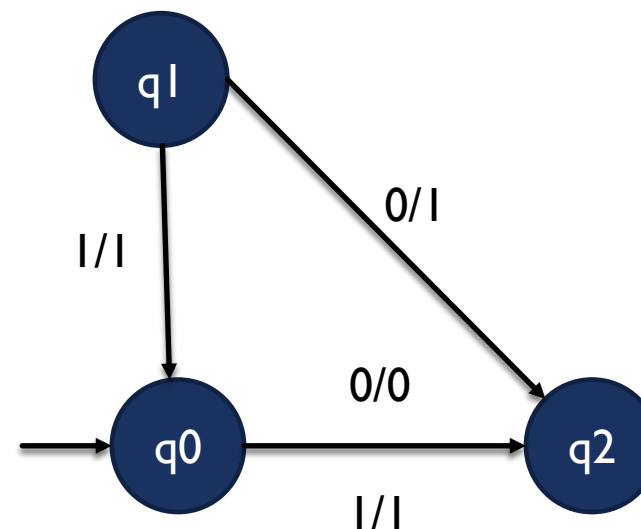

AT STATE Q2, WHEN $A = 1$ AND $B = 0$ AND INPUT = 0


If we are in state q_2 and we receive the input 0:

new $B = \text{old } A = 1$

new $A = 0 \text{ NAND } (1 \text{ OR } 0) = 1$

output = $0 \text{ OR } 0 = 0$

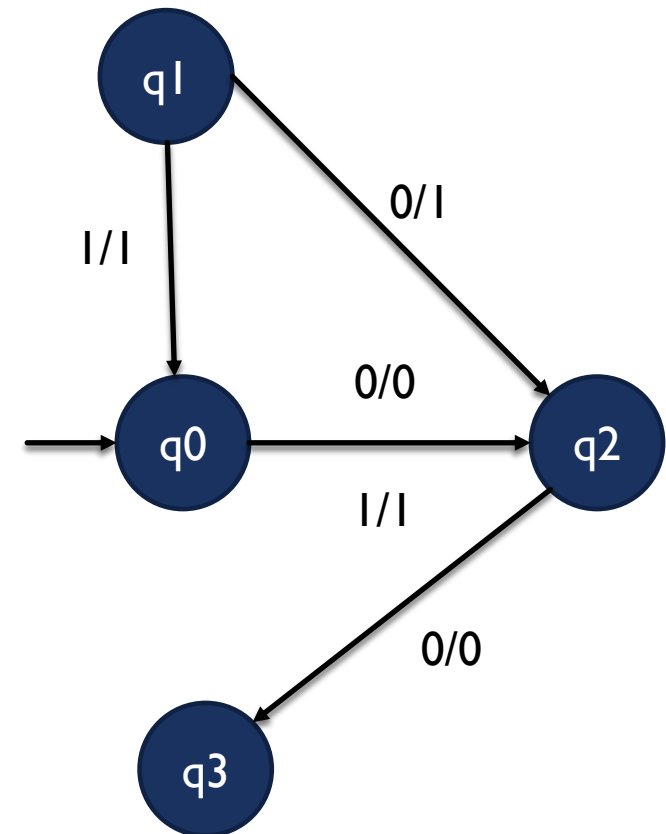The new state is q_3 (since new $A = 1$, new $B = 1$).



AT STATE Q2, WHEN $A = 1$ AND $B = 0$ AND INPUT = 1


If we are in q_2 and we receive the input 1:

$\text{newB} = \text{oldA} = 1$

$\text{newA} = 1 \text{ NAND } (1 \text{ OR } 0) = 0$


$\text{output} = 1 \text{ OR } 0 = 1$

The new state is q_1 .

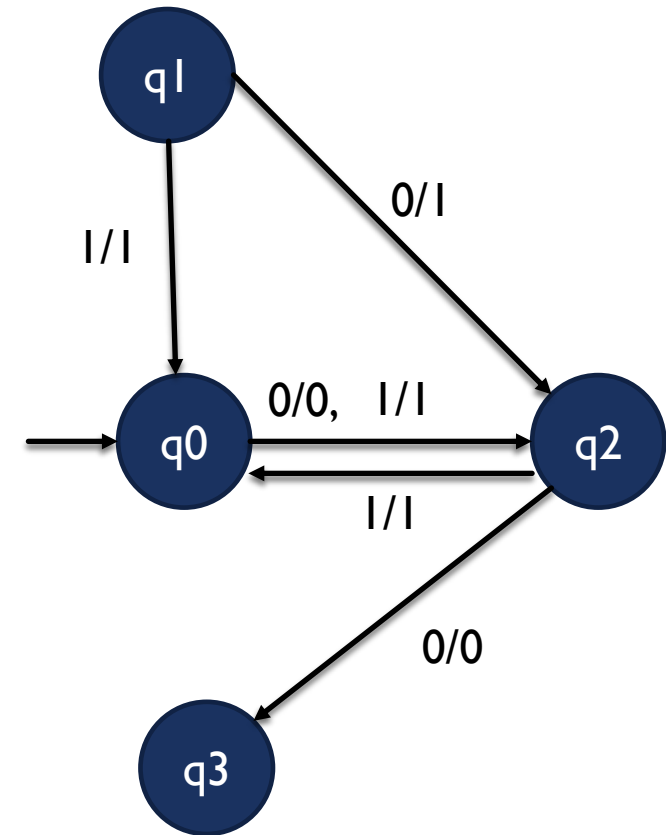

AT STATE Q3, WHEN $A = 1$ AND $B = 1$ AND INPUT = 0

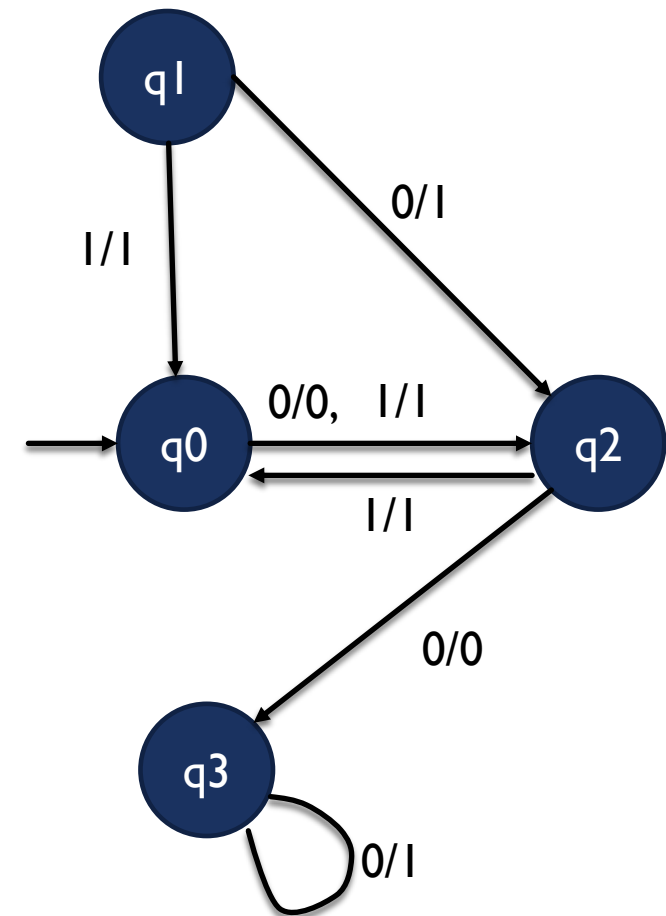- If we are in $q3$ and we receive the input 0:
- $\text{newB} = \text{oldA} = 1$
- $\text{newA} = 0 \text{ NAND } (1 \text{ OR } 1) = 1$
- $\text{output} = 0 \text{ OR } 1 = 1$
- The new state is $q3$.



AT STATE Q3, WHEN $A = 1$ AND $B = 1$ AND INPUT = 1


If we are in q_3 and we receive the input 1:

new $B = \text{old } A = 1$

new $A = 1 \text{ NAND } (1 \text{ OR } 1) = 0$

output = $1 \text{ OR } 1 = 1$

The new state is q_1

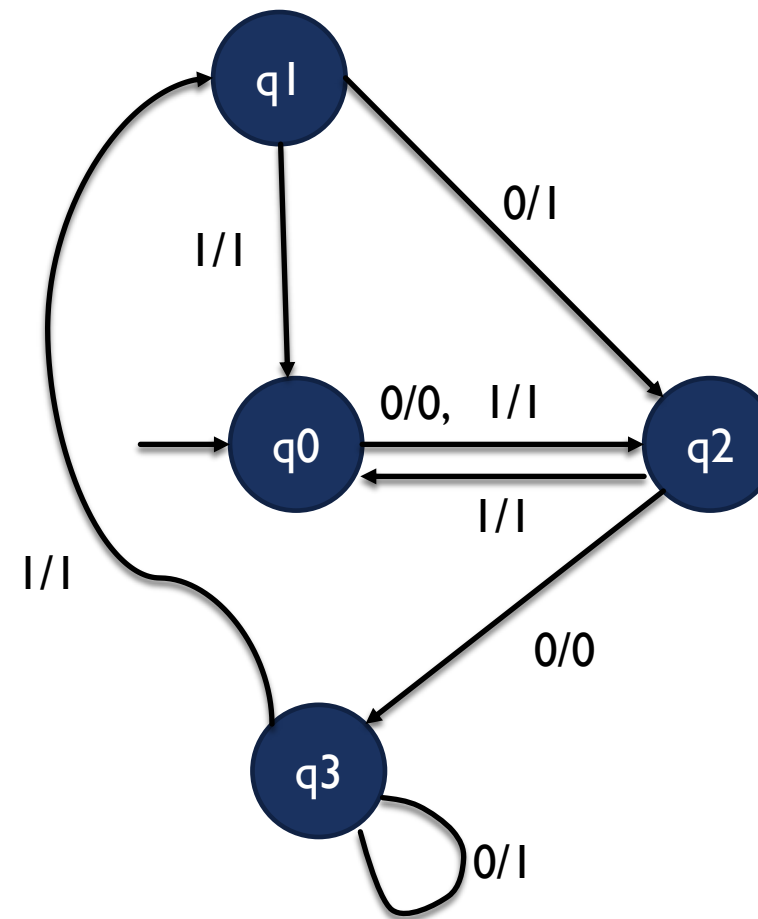

FINAL TRANSITION TABLE

Old State	After Input 0		After Input 1	
	New State	Output	New State	Output
Q0	Q2	0	Q2	1
Q1	Q2	1	Q0	1
Q2	Q3	0	Q1	1
Q3	Q3	1	Q1	1

- If we input two 0's no matter which state we started from, we will get to state q3.
- From there the input string **011011** will cause the output sequence **111011**.

